3. Due to the high current flow in the armature, which of the following effect does not occur?
   a. Over heat
   b. Sparking
   c. Voltage drop
   d. Increase in efficiency

4. In which DC motor, the three point starter is used
   a. Shunt motor
   b. Compound motor
   c. Shunt and compound motor
   d. Series motor

5. The terminal of the three point starter is
   a. Line, Armature, Field coil
   b. Line, Resistance, Field coil
   c. Armature, Field coil, Resistance
   d. Resistance, Line, Armature

6. The protective devices used in the three point starters are
   a. No volt release coil
   b. Over load release coil
   c. No volt and over load release coil
   d. Electromagnet coil

7. What should be done to obtain the increase speed in three point starter?
   a. Increase resistance value
   b. Field current value should be change
   c. Decrease resistance value
   d. Voltage should be maintained

8. In four point starter, how the no volt release coil should be connected with field coil.
   a. in series
   b. in shunt
   c. directly
   d. parallel

9. The current taken by the induction motor in the order of ------- times that of full load current at starting time.
   a. 1 to 8
   b. 5 to 8
   c. 1 to 10
   d. 5 to 10

10. Induction motor is operated with full voltage in
   a. Star-delta starter
   b. Rotor resistance starter
   c. Direct-on-line starter
   d. Auto-transformer starter

11. ---------- induction motor is operated with low voltage.
   a. Direct-on-line and auto transformer starter
   b. Star-delta and rotor resistance starter
   c. Star-delta and auto transformer starter
   d. Direct-on-line and rotor resistance starter

12. In which starter, the starting current is reduced to one – third value?
   a. Direct-on-line starter
   b. Star delta starter
   c. Rotor resistance starter
   d. Auto transformer starter

13. Electrical isolator should be used in ---------- condition.
   a. No load
   b. With load
   c. With less load
   d. With very high load

14. Electrical circuit breaker is like a ----------
   a. resistance
   b. capacitance
   c. switch
   d. inductance

BEE_ENG_Chapter_08.indd 130 12/27/2019 10:59:55 AM