PART–C

Answer the questions in one page **(5 Marks)**

1. State the necessity of starters in DC motor with example.
2. Draw the circuit diagram of four point starter.
3. With a neat sketch, explain the operation of auto-transformer starter.
4. Compare the different types of electrical circuit breaker.
5. Explain the different types of miniature circuit breaker.
6. Explain the operation of voltage operated earth leakage circuit breaker.

PART–D

Answer the questions in two page **(10 Marks)**

1. Explain the construction and operation of three point starter with a neat sketch.
2. With a neat diagram, explain the construction and working principle of star-delta starter.
3. Explain the construction and operation of direct-on-line starter with a neat sketch.

Reference Book

1. A text book of 'Electrical Technology' Volume-III B.L.Theraja and A.K.Theraja, S.Chand & Company Ltd.

Reference Internet Source

1. http://www.wikipedia.org
2. https://www.electrical4u.com

BEE_ENG_Chapter_08.indd 132 12/27/2019 10:59:55 AM