Practical 7

Measurement of energy of the given electrical equipment

AIM


To measure the energy of the given electrical equipment (pure resistive load).

Apparatus required

S.No.	Equipment Required	Quantity
1	Voltmeter	1
2	Ammeter	1
3	Electrical equipment (lamp load)	1
4	ICDP switch	1
5	Connecting wire	as required

Procedure

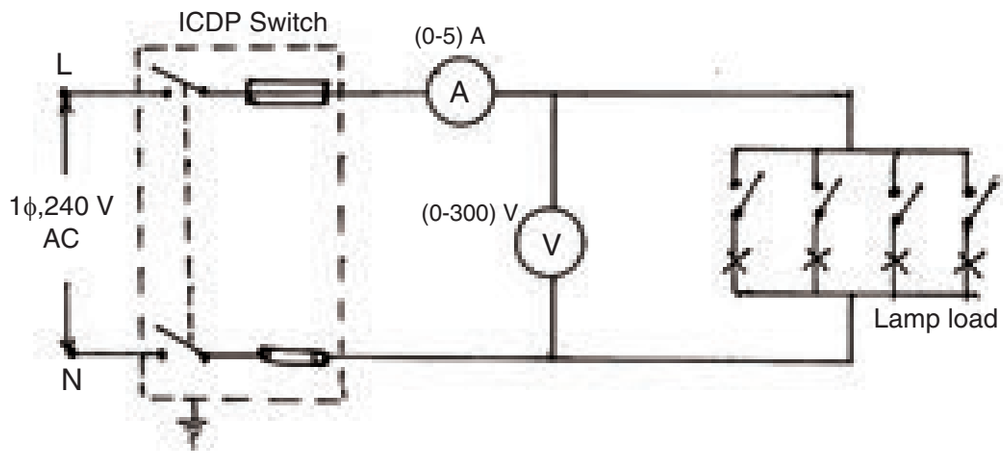1. Connections are made as per the circuit diagram.
2. After checking the connections, close the ICDP switch.
3. Note down the readings of voltmeter and ammeter.
4. Switch off the supply after 5 minutes.
5. Calculate the energy consumed.



BEE_ENG_Pratical.indd 193 12/27/2019 10:54:35 AM