Practical 8


Determination of winding resistance by Ammeter- Voltmeter method

AIM

To determine the value of winding resistances of starting and running windings of the given AC, single phase capacitor type Induction motor by Ammeter – Voltmeter method.

Instruments and materials required

Sl. No.	Apparatus	Type	Quantity
1	Capacitor type induction motor	-	1
2	Ammeter	(0-10A) M.C type	1
3	Voltmeter	(0-30V) M.C type	1
4	Rheostat	50Ω	1
5	Line tester	-	1
6	Cutting plier	-	1
7	Screw driver	-	1
8	1/18 SWG connecting wires	-	Sufficient length

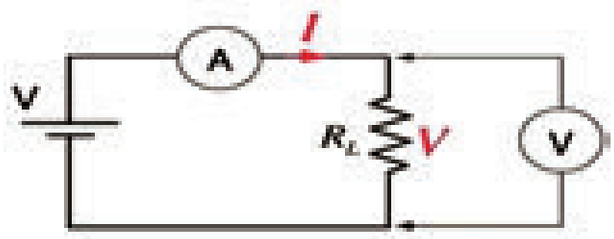

$$R_L = \frac{V}{I}$$

BEE_ENG_Pratical.indd 195 12/27/2019 10:54:35 AM