Procedure

i. Connections are made as shown in the figure and the supply is given.
ii. Starting winding is connected first with the circuit to find its resistance value.
iii. The voltage applied and current through the starting winding is measured by voltmeter and ammeter respectively and tabulated.
iv. Similarly running winding is connected with the circuit. Then voltmeter and ammeter readings are noted and tabulated.
v The average resistance value of the starting and running winding is calculated and compared with the original values.
vi. If the calculated average value of resistance is equal to the original values, there is no short circuit in the windings and if it is low, then there will be a short circuit in the concerned winding.

Table for starting winding

Sl. No.	Voltmeter reading (V)	Ammeter reading (I)	Resistance R = V/I
1			
2			
3			
Total resistance value			

Average resistance value of the starting winding

$$R_{av} = \frac{Total\ Resistance\ value\ (R_T)}{No.\ of\ readings\ taken}$$

Table for running winding

Sl. No.	Voltmeter Reading (V)	Ammeter Reading (I)	Resistance R = V/I
1			
2			
3			
Total resistance value			

BEE_ENG_Pratical.indd 196 12/27/2019 10:54:35 AM