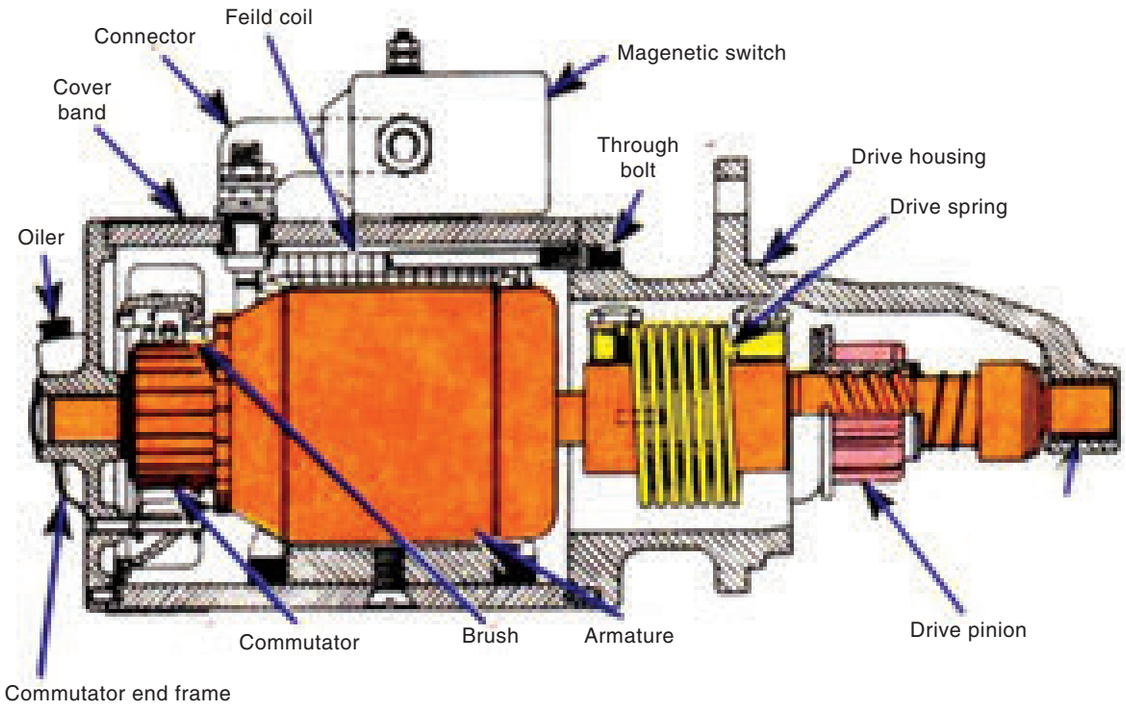


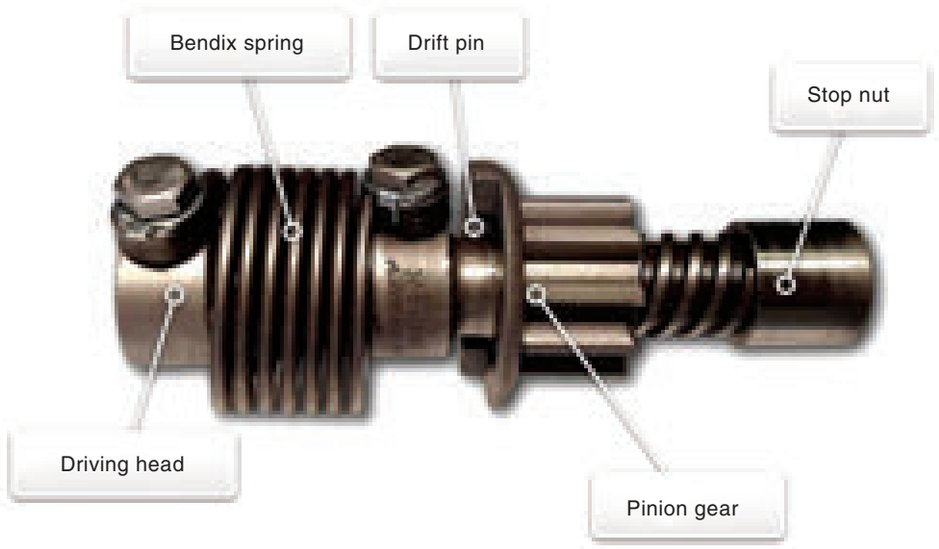


Figure 10.8.1.1 (a) Bendix drive starting system

10.8.2 Starting switch

The switch is a device which is used to open and close the electric circuit. A starting switch is used between the starter motor and the battery. In this, plunger, contact disc, pull-in – windings, terminals and connection wires are there. When the switch is on, the current passes from the battery to the pull-in – windings and it get magnetised. It pulls the contact disc and closes the circuit between the battery and the starter motor. When the switch is off, the pull-in – windings get demagnetise and the spring makes the circuit open between the battery and the starter motor. It is also called as 'Solenoid Switch'.

BAE_ENG_Chapter_10.indd 201 12/20/2019 1:10:25 PM